A rectangular area with a dark green, marbled or textured background, containing white text.

# EE-101-2020 Week- 1 Assignment

# Question

1. (a) Identify the first five harmonics of the square wave  $v(t)$  expressed in the Fig 1. Consider  $V = +2$  Volt,  $T = 628$  msec

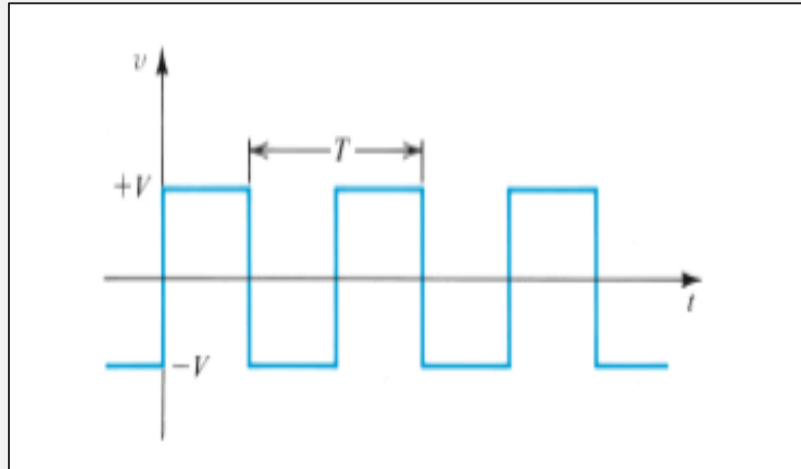


Fig. 1

- (b) What fraction of energy of  $v(t)$  is in its fundamental?
- (c) What fraction of energy of  $v(t)$  is in its first five harmonics?
- (d) Till what number of harmonics is 90% of the energy?

## Question

2. (a) Find the time period. and the cyclic and radian frequencies for each of the following sinusoids

$$v_1(t) = 17 \cos(2000t - 30^\circ)$$

$$v_2(t) = 12 \cos(2000t + 30^\circ)$$

(b) Derive the expression and sketch the graph of  $v_3(t) = v_1(t) + v_2(t)$   
[Graph Paper Preferred]

## Question

3. Graphically sketch the waveform described by

$$v(t) = \frac{r(t)}{T_c} \left[ V_A e^{-\frac{t}{T_c}} \right] u(t) \text{ Volt}$$

[Graph Paper Preferred]

$$V_A = 1 \text{ Volt}, \quad T_c = 1 \text{ sec}$$

## Question

4. (a) Express the Gated Pulse Waveform of Fig.2 in terms of Step functions  $u(t)$ .

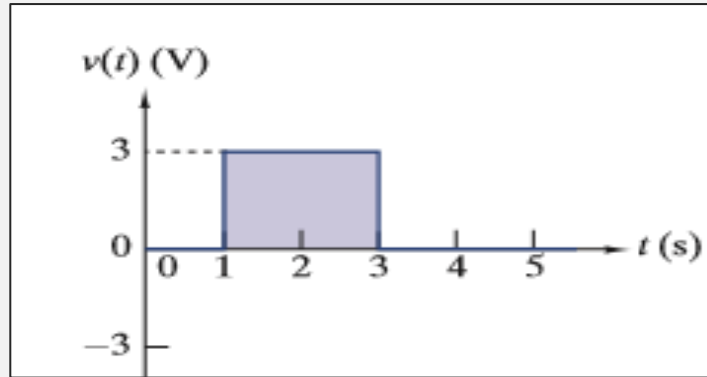


Fig. 2

(b) Determine the expression and graphically sketch the derivative of the gated pulse waveform shown in Fig.2 [Graph Paper Preferred]

(c) Determine the expression and graphically sketch the integral of the gated pulse waveform shown in Fig.2 [Graph Paper Preferred]

## Question

5. (a) Plot  $v(t)$  expressed by

$$v(t) = 10[e^{-1000t} - e^{-2500t}]u(t)$$

[Graph Paper Preferred]

(b) What is the value of  $v(t)$  at the extremum and the time when it occurs?

## Question

6. Find the equivalent resistance seen from terminal A-B using Y -  $\Delta$  transformation in Fig. 3  $R_L = 10\ \Omega$

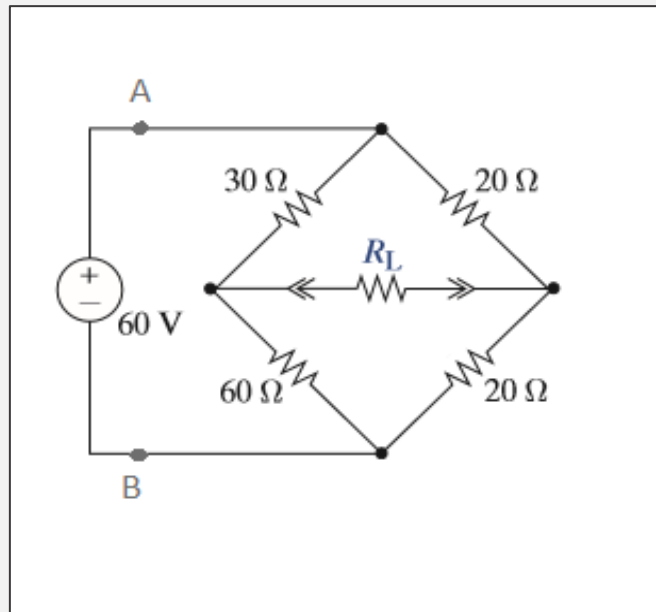


Fig. 3

## Question

7. The graph in Fig.4 shows the charge  $q(t)$  flowing past a point in a wire as a function of time

(a) Sketch the variation of  $i(t)$  versus time [Graph paper preferred]

(b) Find the current  $i(t)$  at 1; 2.5; 3.5; 4.5, and 5.5 msec

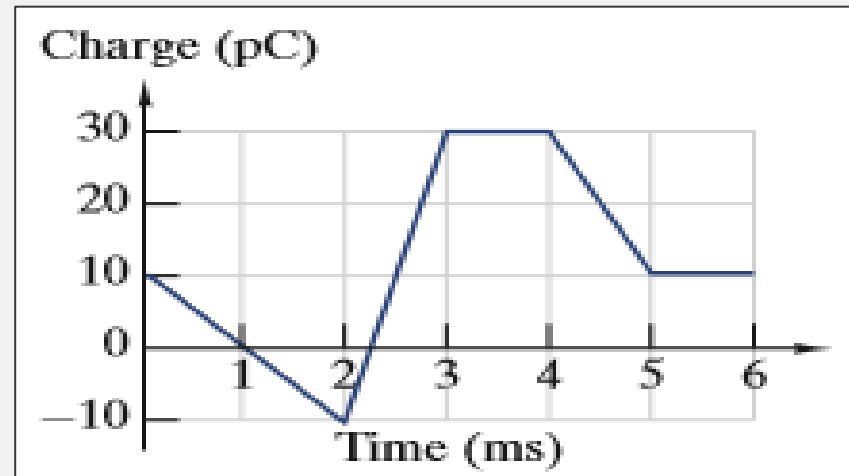


Fig. 4



## Question

8. Figure 5 shows the voltage across a  $0.5\text{-}\mu\text{F}$  capacitor. Determine the time varying current, energy and power of the capacitor [Graph Paper Preferred]

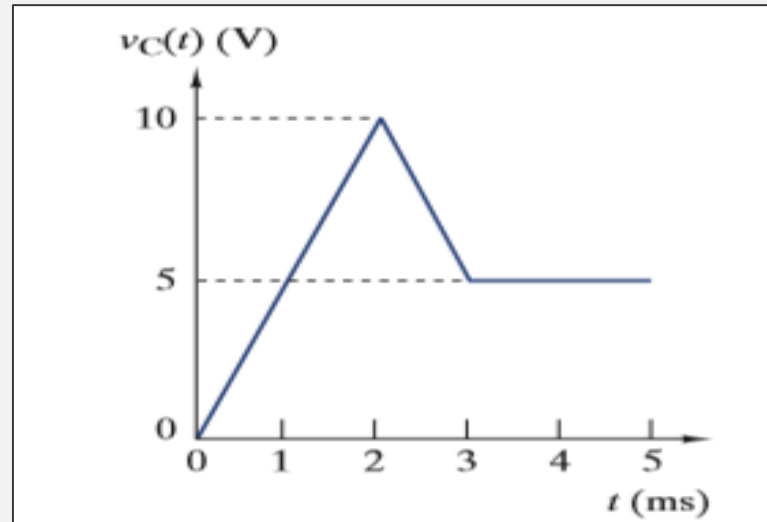


Fig. 5

## Question

9. The current through a 2.5-mH inductor

$$i(t) = 10 \cdot (e^{-500t}) \cdot (\sin 2000t)$$

Plot the waveforms of the element current, voltage, power, and energy. [Graph Paper Preferred]

# Question

10. For the first-order low pass filter as shown below,

(a) Draw s-domain transformed circuit for the filter.

(b) Find transfer function in s-domain i.e  $T(s) = \frac{V_o(s)}{V_i(s)}$ .

(c) Hence find transfer function for physical frequencies i.e  $T(j\omega)$  by  $s = j\omega$  and derive expression for magnitude response,  $|T(j\omega)|$


(d) Also calculate the 3-dB frequency or corner frequency,  $\omega_o$  for the filter.

(e) Find the transmission or gain at  $\frac{\omega}{\omega_o} = 0.1$ ,  $\frac{\omega}{\omega_o} = 1$  and at  $\frac{\omega}{\omega_o} = 10$

(f) Plot magnitude response,  $|T(j\omega)|$  vs.  $\frac{\omega}{\omega_o}$

Assume that the capacitor is at a zero state initially

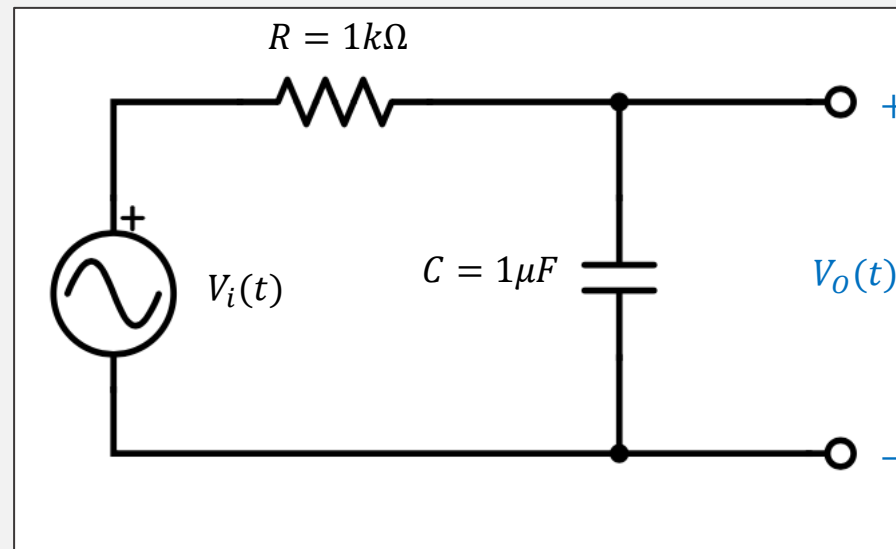i.e.  $V_C(t = 0) = V(t = 0) = 0 \text{ V}$



# Question

11. For the first-order  $R$ - $L$  circuit as shown below,

(a) Draw s-domain transformed circuit for the filter.

(b) Find transfer function in s-domain i.e  $T(s) = \frac{V_o(s)}{V_i(s)}$ .


(c) Hence find transfer function for physical frequencies i.e  $T(j\omega)$  by  $s = j\omega$  and derive expression for magnitude response,  $|T(j\omega)|$

(d) Also calculate the 3-dB frequency or corner frequency,  $\omega_o$  for the filter.

(e) Find the transmission or gain at  $\frac{\omega}{\omega_o} = 0.1$ ,  $\frac{\omega}{\omega_o} = 1$  and at  $\frac{\omega}{\omega_o} = 10$

(f) Plot magnitude response,  $|T(j\omega)|$  vs.  $\frac{\omega}{\omega_o}$

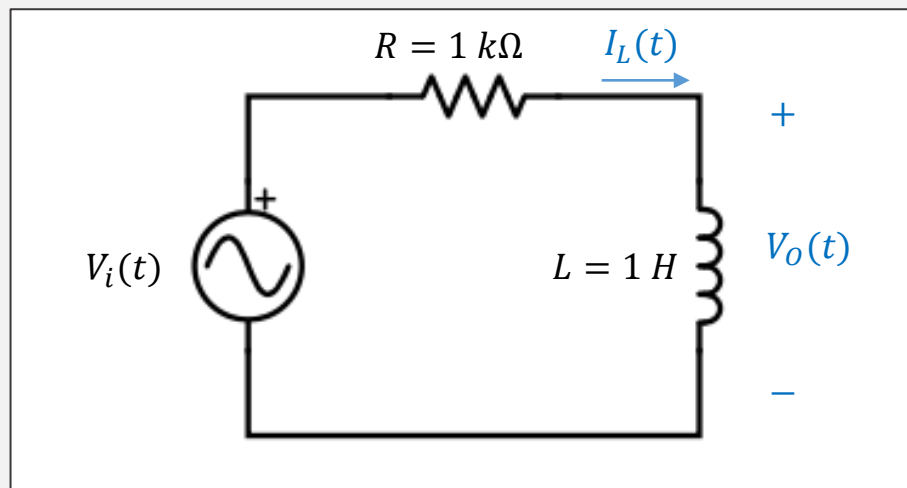Assume that the inductor is at zero state initially i.e.  $I_L(t = 0) = 0$  A.



# Question

12. For a second-order low pass filter derived by cascading two first order RC low pass filter stage as shown below,

(a) Draw s-domain transformed circuit for the filter.

(b) Find transfer function in s-domain for Stage (I), Stage (II) and overall transfer function i.e.  $T_I(s) = \frac{V_X(s)}{V_I(s)}$ ,  $T_{II}(s) = \frac{V_O(s)}{V_X(s)}$  and  $T(s) = \frac{V_O(s)}{V_i(s)}$  respectively


(c) Hence find transfer function for physical frequencies i.e  $T(j\omega)$  by  $s = j\omega$  and derive expression for magnitude response,  $|T(j\omega)|$

(d) Also calculate the corner frequency,  $\omega_o$  for the filter.

(e) Find the transmission or gain at  $\frac{\omega}{\omega_o} = 0.1$ ,  $\frac{\omega}{\omega_o} = 1$  and at  $\frac{\omega}{\omega_o} = 10$

(f) Plot magnitude response,  $|T(j\omega)|$  vs.  $\frac{\omega}{\omega_o}$

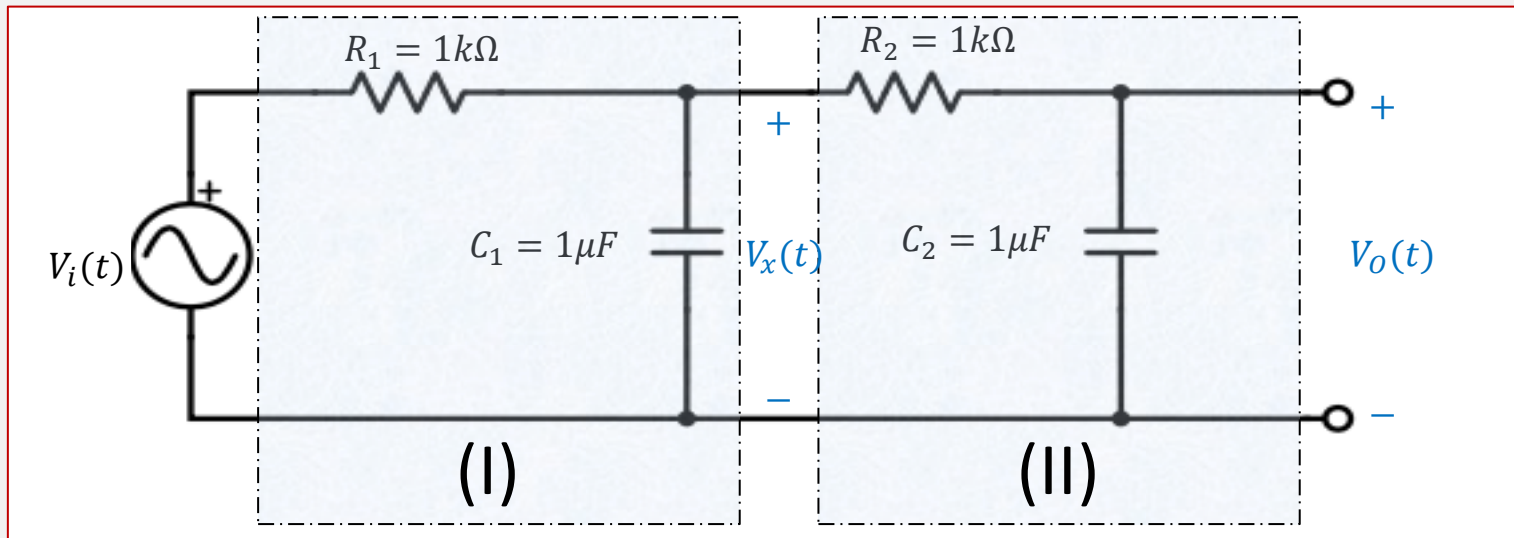Assume that the capacitor is at a zero state initially i.e.  $V_{C_1}(t = 0) = V_{C_2}(t = 0) = 0$  V, also  $R_1 = R_2$ ,  $C_1 = C_2$



# Question

13. For the second-order series  $R$ - $L$ - $C$  resonator circuit as shown below,

(a) Draw s-domain transformed circuit for the resonator

(b) Find impedance offered by the circuit in s-domain i.e.  $Z(s) = \frac{V_I(s)}{I_I(s)}$

(c) Hence find impedance for physical frequencies i.e.  $Z(j\omega)$  by considering  $s = j\omega$  and derive expression for magnitude response,  $|Z(j\omega)|$

(d) Determine the resonant frequency,  $\omega_o$  where the circuit offers purely resistive impedance

(e) Plot  $|Z(j\omega)|$  and  $|Y(j\omega)| = \frac{1}{|Z(j\omega)|}$  versus normalised frequency,  $\frac{\omega}{\omega_o}$

Assume that the inductor and capacitor are at zero state initially i.e.  $I_L(t = 0) = 0$  A and  $V_C(t = 0) = 0$  V

